

DLD LAB WIN_2021

LAB-2

Aim: To simulate different types of logic gates of full adder, half subtractor, full subtractor.

Tools used: vivado software

Truth tables:

- Full adder:

A	B	C	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Half subtractor:


A	B	SUM	CARRY
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

- Full subtractor:


A	B	C	borrow	difference
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Circuit diagrams:


Full adder:

 

Half subtractor:

 

Full subtractor:

 

Codes:


Full adder:



```
C:/Users/91995/full_adder_14mar2021/full_adder_14mar2021.srcs/sources_1/new/fulladder.v
1 `timescale 1ns / 1ps
2 //////////////////////////////////////////////////
3 // Company:
4 // Engineer:
5 //
6 // Create Date: 19.03.2021 22:51:10
7 // Design Name:
8 // Module Name: fulladder
9 // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 //////////////////////////////////////////////////
21
22
23 module fulladder(x,y,z,sum,carry);
24 input x,y,z;
25 output sum,carry;
26 wire sum1 , carry1,carry2;
27
28 halfadder x1(x,y,sum1,carry1);
29 halfadder a1(sum1,z,sum,carry2);
30 xorgate_behavioral b1(carry1,carry2,carry);
31 endmodule
32
```



Test bench code:


```
C:/Users/91995/full_adder_14mar2021/full_adder_14mar2021.srcs/sim_1/new/tb_fulladder.v
1  `timescale 1ns / 1ps
2  //////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
3  // Company:
4  // Engineer:
5  //
6  // Create Date: 19.03.2021 22:53:37
7  // Design Name:
8  // Module Name: tb_fulladder
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 //////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
21
22
23 module tb_fulladder;
24   reg x,y,z;
25   wire sum,carry;
26
27   fulladder bl(x,y,z,sum,carry);
28
29   initial
30   begin
31     x = 0;y=0;z=0;
32     #1 x = 0;y = 0;z = 0;
33     #1 x = 0;y = 0;z = 1;
34     #1 x = 0;y = 1;z = 0;
35     #1 x = 0;y = 1;z = 1;
36     #1 x = 1;y = 0;z = 0;
37     #1 x = 1;y = 0;z = 1;
38     #1 x = 1;y = 1;z = 0;
39     #1 x = 1;y = 1;z = 1;
40
41   end
42 endmodule
```

Outputs:

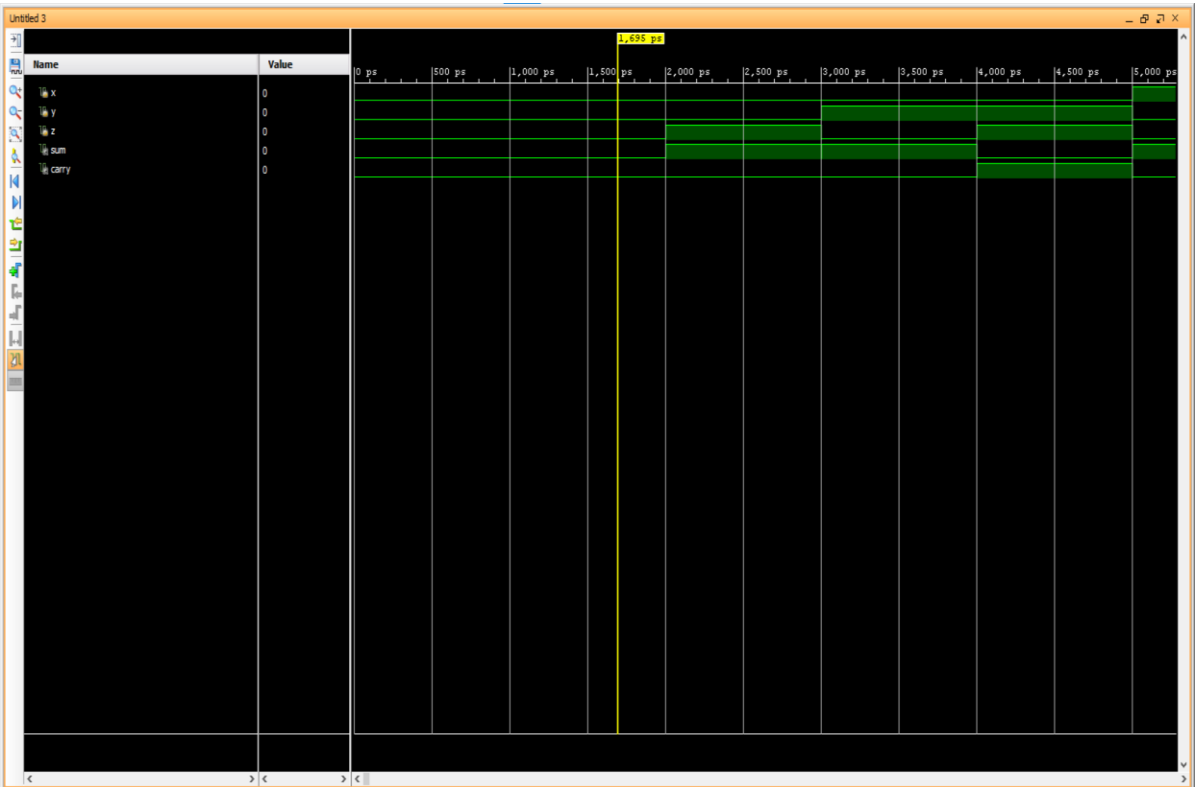

  

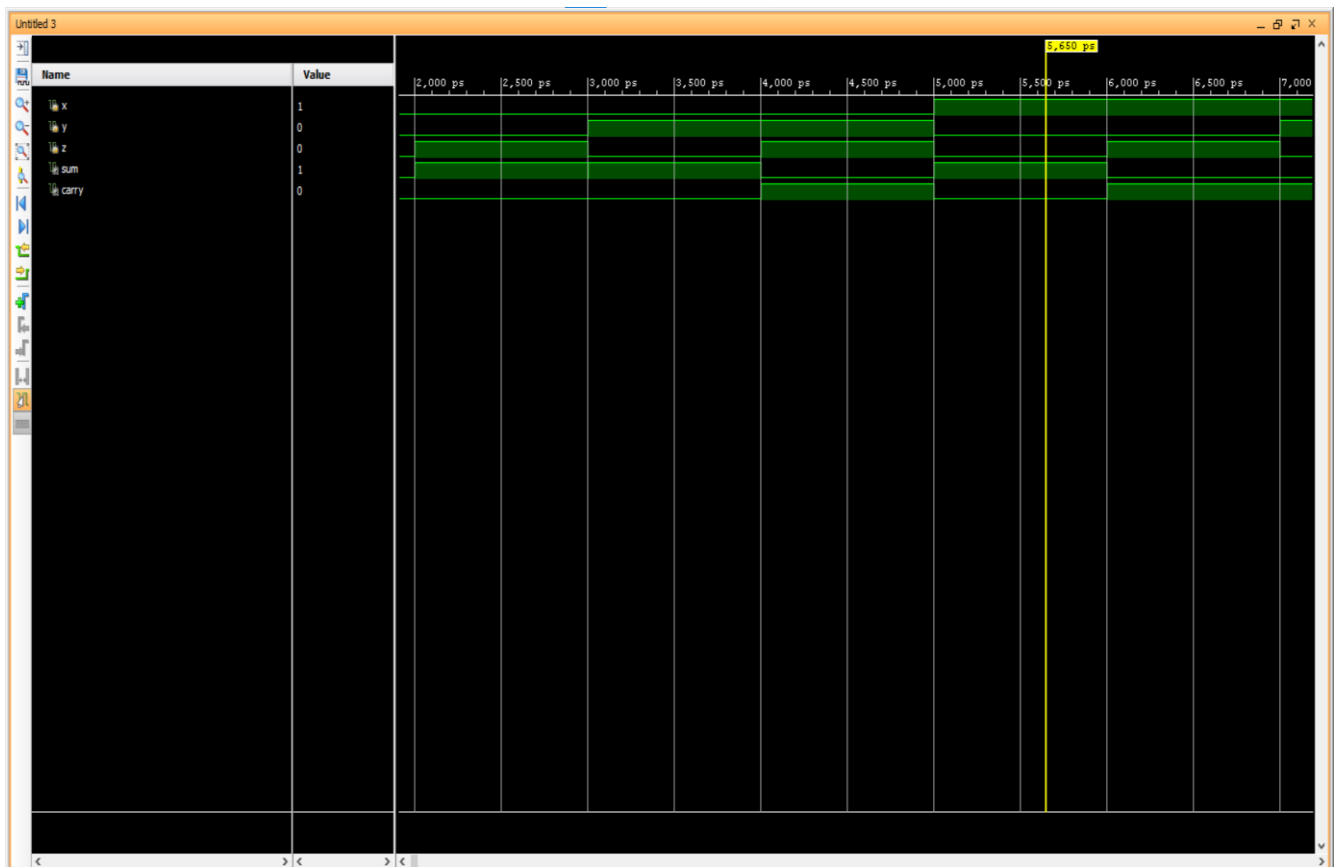 

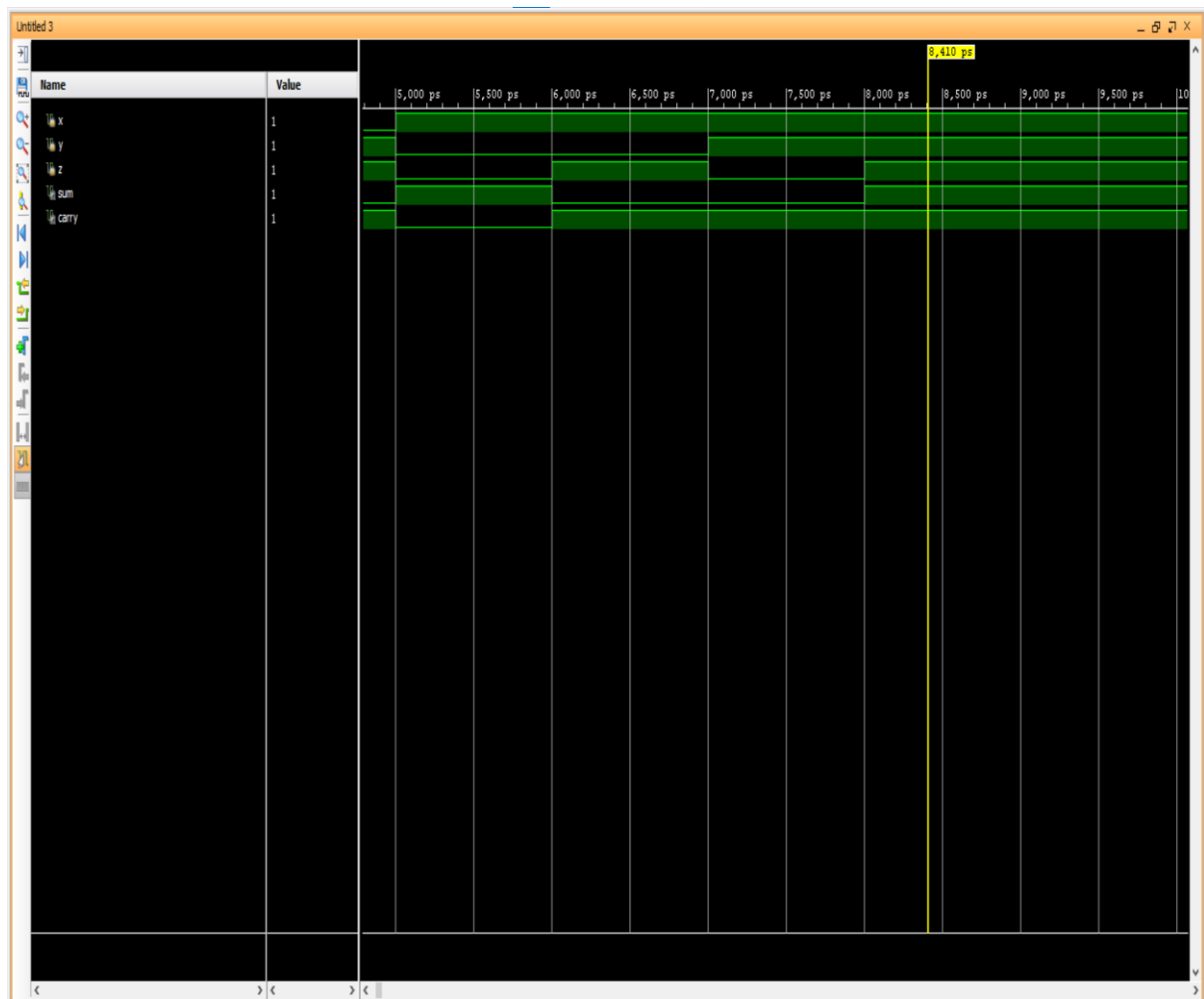

Half subtractor:


C:/Users/91995/halfsubractor/halfsubractor.srscs/sources_1/new/halfsubractor.v


```
1 `timescale 1ns / 1ps
2 ///////////////////////////////////////////////////
3 // Company:
4 // Engineer:
5 //
6 // Create Date: 19.03.2021 22:38:06
7 // Design Name:
8 // Module Name: halfsubractor
9 // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////
21
22
23
24 module halfSubractor(X,Y,Diff,Borr);
25 input X, Y;
26 output Diff, Borr;
27 ○ assign Diff = X ^ Y;
28 ○ assign Borr = ~X & Y;
29 endmodule
30
31
```

Test bench code:

```
C:/Users/91995/halfsubractor/halfsubractor.srscs/sim_1/new/tb_halfsubractor.v
1  `timescale 1ns / 1ps
2  //////////////////////////////////////
3  // Company:
4  // Engineer:
5  //
6  // Create Date: 19.03.2021 22:38:29
7  // Design Name:
8  // Module Name: tb_halfsubractor
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 //////////////////////////////////////
21
22
23 module tb_halfSubractor;
24   reg X, Y;
25   wire Diff, Borr;
26
27   halfSubractor h1(X,Y,Diff,Borr);
28   initial begin
29     X = 0; Y = 0;
30     #1 X = 0; Y = 1;
31     #1 X = 1; Y = 0;
32     #1 X = 1; Y = 1;
33   end
34 endmodule
```

Outputs:

 

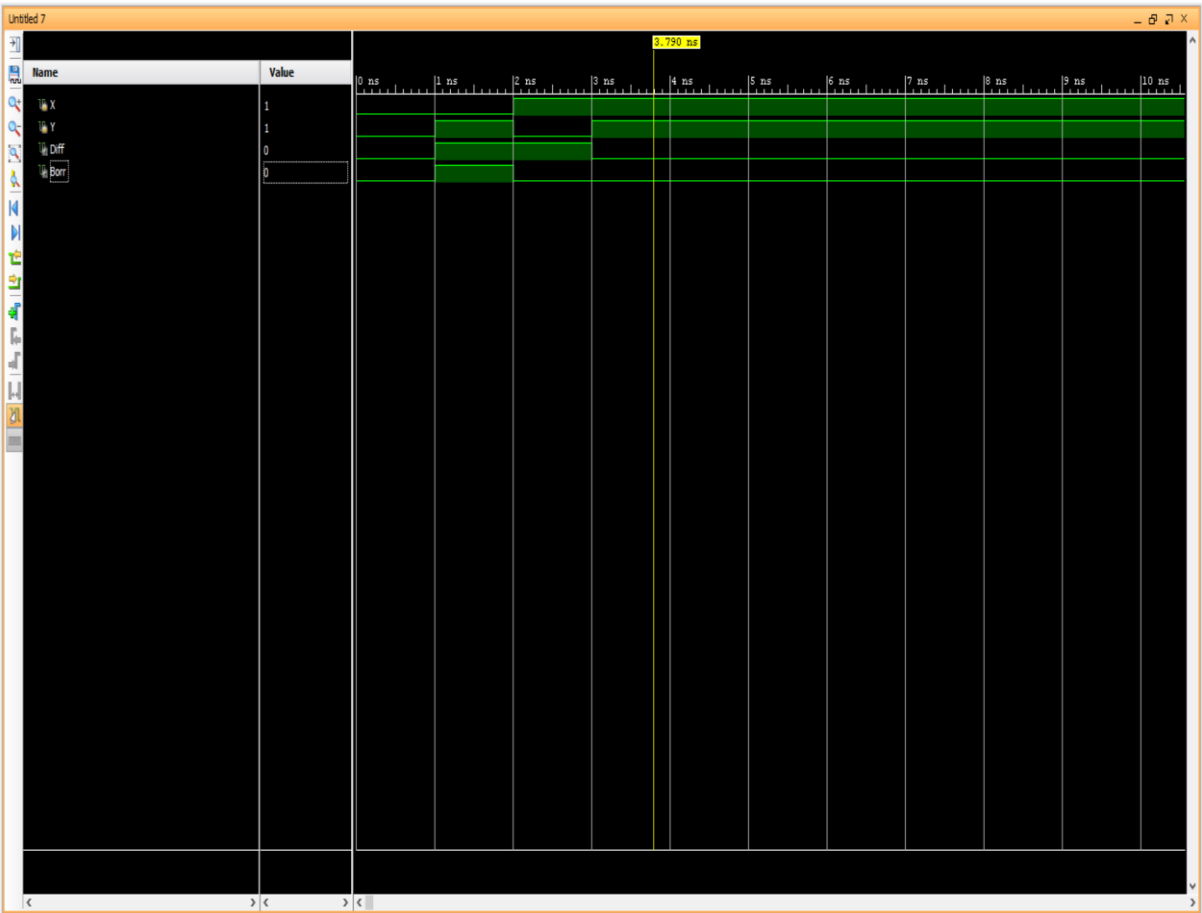

Full subtractor:

```
module fullsubtractor(A,B,C,Diff,Borr);  
input wire A, B, C;  
output reg Diff,Borr;  
always @(A or B or C)  
begin  
    if(A==0 && B==0 && C==0)  
        begin  
            Diff=0;  
            Borr=0;  
        end  
    else if(A==0 && B==0 && C==1)  
        begin  
            Diff=1;  
            Borr=1;  
        end  
    else if(A==0 && B==1 && C==0)  
        begin  
            Diff=1;  
            Borr=1;  
        end  
    else if(A==0 && B==1 && C==1)  
        begin  
            Diff=0;  
            Borr=1;  
        end  
    else if(A==1 && B==0 && C==0)
```



```
begin
    Diff=1;
    Borr=0;
end
else if(A==1 && B==0 && C==1)
begin
    Diff=0;
    Borr=0;


end
else if(A==1 && B==1 && C==0)
begin
Diff=0;
    Borr=0;
end
else if(A==1 && B==1 && C==1)
begin
    Diff=1;
    Borr=1;
end
end
endmodule
```


Test bench code:

```
1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Company:
4  // Engineer:
5  //
6  // Create Date: 19.03.2021 23:31:37
7  // Design Name:
8  // Module Name: tb_fullsubtractor
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23
24 module tb_fullsubtractor;
25 reg A,B,C;
26 wire Diff, Borr;
27 fullsubtractor f1(A,B,C,Diff,Borr);
28 initial
29 begin
30     A = 0; B = 0; C = 0;
31     #1 A = 0; B = 0; C = 1;
32     #1 A = 0; B = 1; C = 0;
33     #1 A = 0; B = 1; C = 1;
34     #1 A = 1; B = 0; C = 0;
35     #1 A = 1; B = 0; C = 1;
36     #1 A = 1; B = 1; C = 0;
37     #1 A = 1; B = 1; C = 1;
38 end
39 endmodule
```


Outputs:

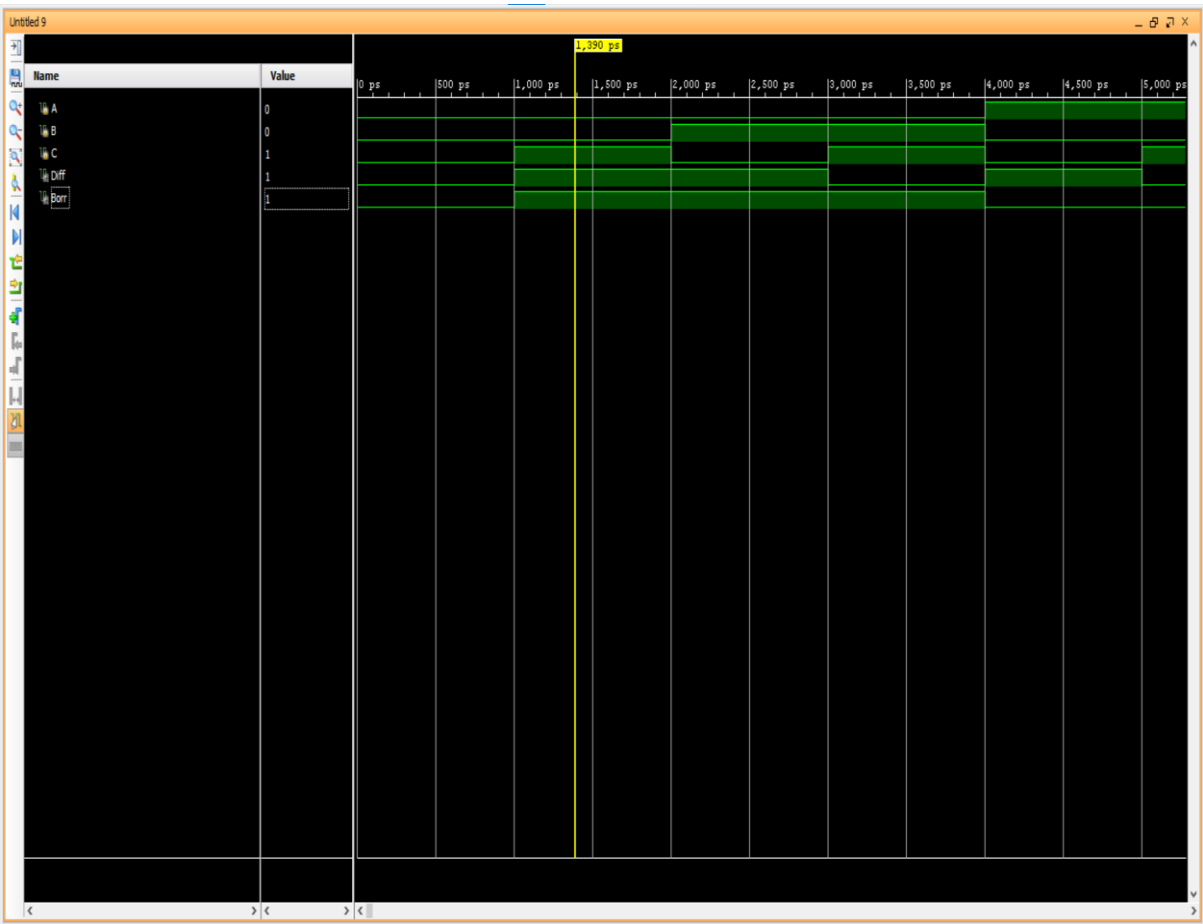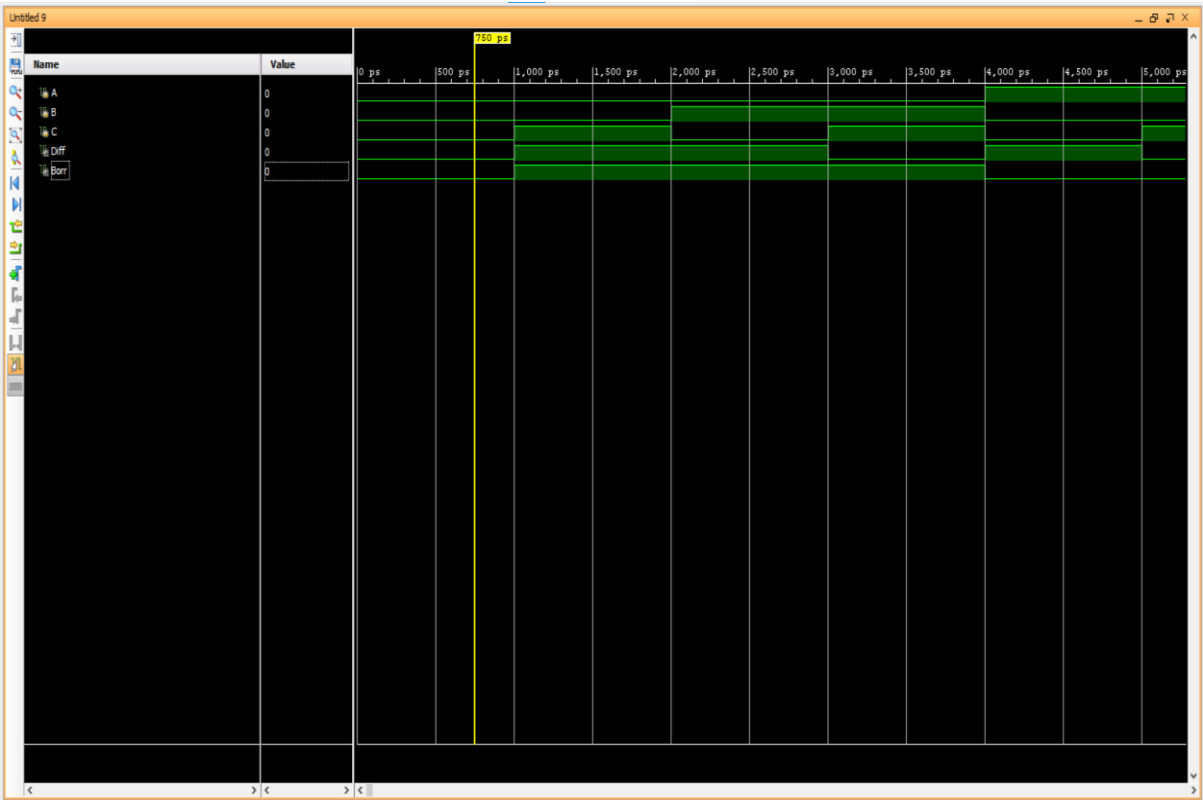

 

 

Conclusion:

There are three different types of modelling styles

1. Dataflow
2. Structural
3. Behavioral

With these types of modelling styles I have done the simulation of logic gates (full adder, half subtractor, full subtractor)

Now I'm aware of full adder, half subtractor, full subtractor logic gates

Finally, in this lab I came to know about

- Truth tables
- Logic gate diagrams
- Boolean expressions for logic gates
- Different types of modelling
- Output analysis

Reference links:

<https://www.geeksforgeeks.org/>

<https://theorycircuit.com/>