

# DLD

## LAB REPORT


### EXPERIMENT 11

Aim: To simulate the logic gates of 8bit shift registers


Tools used: vivado software

Truth table:

Ring counter(4bit):


| M   | Clk | Q3 | Q2 | Q1 | Q0 |
|---|-----|----|----|----|----|
|  | X   | 0  | 0  | 0  | 1  |
| 1   | ↓   | 0  | 0  | 1  | 0  |
| 1   | ↓   | 0  | 1  | 0  | 0  |
| 1   | ↓   | 1  | 0  | 0  | 0  |
| 1   | ↓   | 0  | 0  | 0  | 1  |
| 1   | ↓   | 0  | 0  | 1  | 0  |

Johnson counter(4bit):


| M   | Clk | Q3 | Q2 | Q1 | Q0 |
|---|-----|----|----|----|----|
|  | X   | 0  | 0  | 0  | 0  |
| 1   | ↓   | 0  | 0  | 0  | 1  |
| 1   | ↓   | 0  | 0  | 1  | 1  |
| 1   | ↓   | 0  | 1  | 1  | 1  |
| 1   | ↓   | 1  | 1  | 1  | 1  |
| 1   | ↓   | 1  | 1  | 1  | 0  |
| 1   | ↓   | 1  | 1  | 0  | 0  |
| 1   | ↓   | 1  | 0  | 0  | 0  |

Diagrams:

Ring counter:

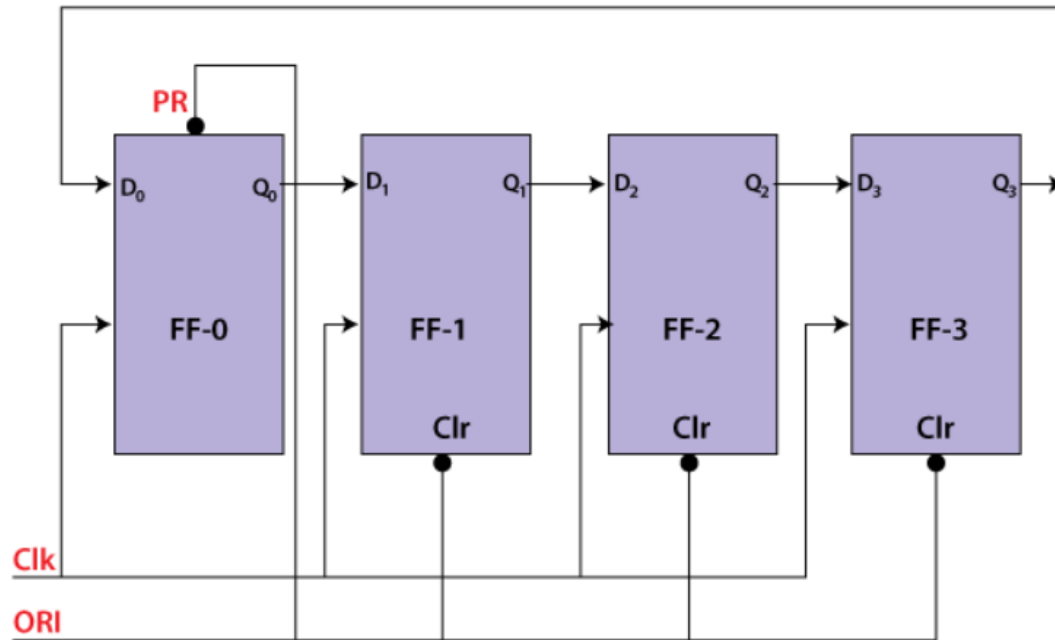

Johnson counter:

 

Codes:

Ring counter:

```
3 module ring_counter(clock,reset,count_out);
4 input clock;
5 input reset;
6 output [3:0]count_out;
7 reg [3:0]count_temp;
8 always@(negedge(clock),posedge(reset))
9 begin
10 if(reset == 1'b1)
11 begin
12 count_temp = 4'b0001;
13 end
14 else if(clock == 1'b1)
15 begin
16 count_temp = {count_temp[2:0],count_temp[3]};
17 end
18 end
19 assign count_out = count_temp;
20 endmodule
```

Testbench code:

```
3 module tb_ring;
4 reg clock;
5 reg reset;
6 wire [3:0]count_out;
7 ring_counter e3(clock,reset,count_out);
8 initial clock = 0;
9 always #10 clock = ~clock;
10 initial begin
11 reset = 1;
12 #50
13 reset = 0;
14 end
15 endmodule
```

## Johnson counter:



```
23 module johnson_counter(clk,reset,Q);
24 input clk,reset;
25 output [3:0] Q;
26 wire d0,d1,d2,d3;
27 not n1(d0,Q[3]);
28 buf b1(d1,Q[0]);
29 buf b11(d2,Q[1]);
30 buf b12(d3,Q[2]);
31 dff A(clk,reset,d0,Q[0]);
32 dff B(clk,reset,d1,Q[1]);
33 dff C(clk,reset,d2,Q[2]);
34 dff D(clk,reset,d3,Q[3]);
35 endmodule
36 module dff(clk,clr,D,Q);
37 input clk,clr,D;
38 output reg Q;
39 always@(negedge clk,posedge clr)
40 begin
41 if(clr)
42 Q<=0;
43 else
44 Q<=D;
45 end
46 endmodule
```



## Testbench code:


```
23 module tb_johnson_counter;
24 reg clk;
25 reg reset;
26 wire [3:0]Q;
27 johnson_counter_15 e3(clk,reset,Q);
28 initial clk = 0;
29 always #10 clk = ~clk;
30 initial begin
31 reset = 1;
32 #50
33 reset = 0;
34 end
35 endmodule
36
```

Results:


Ring counter 4 bit:

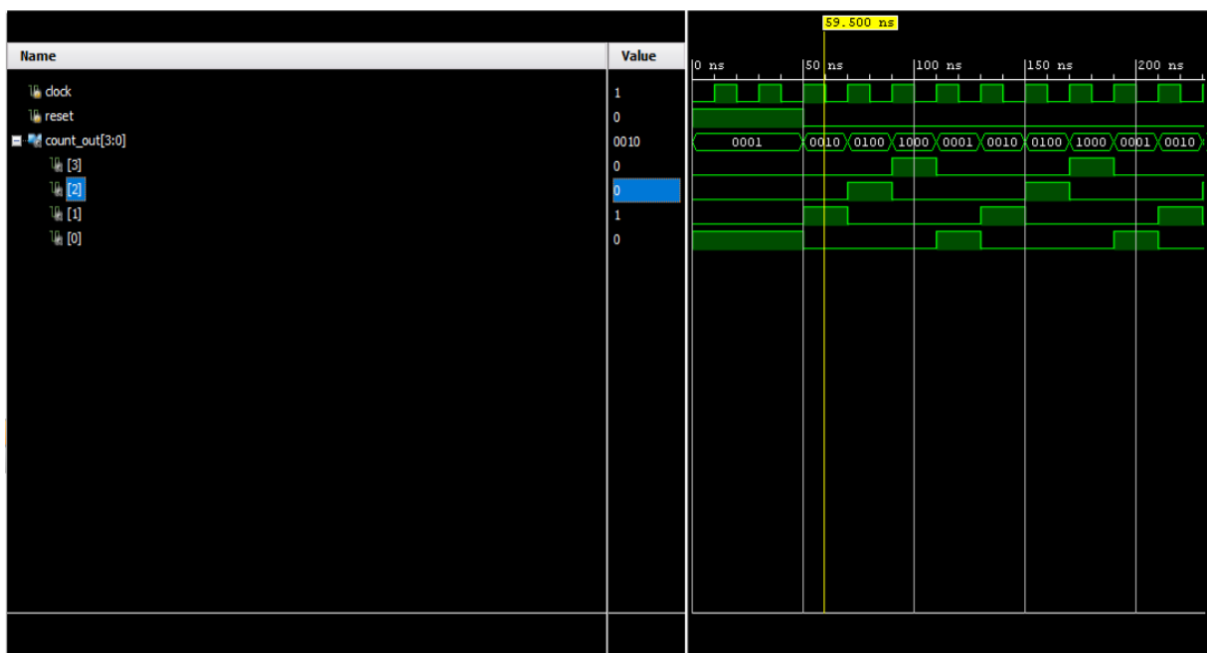
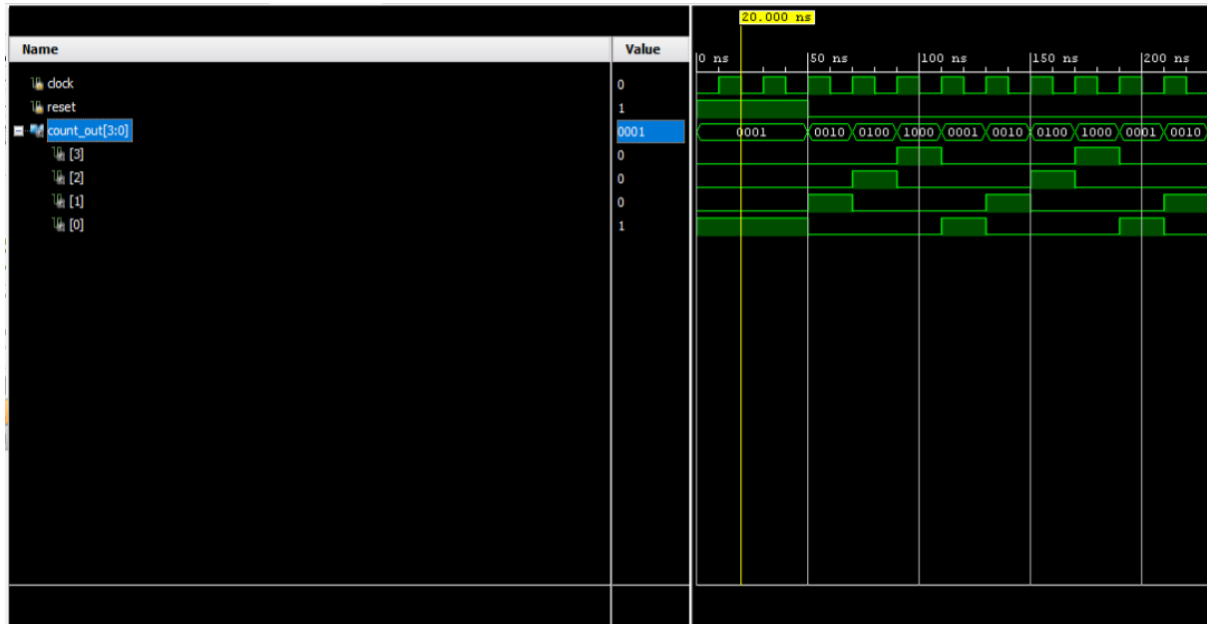


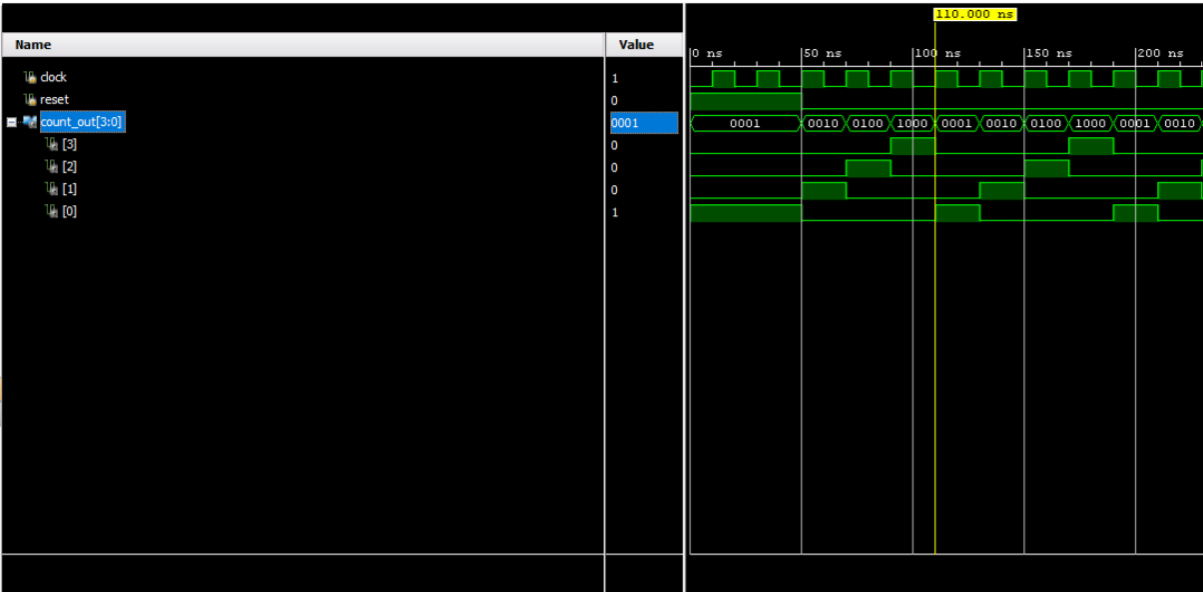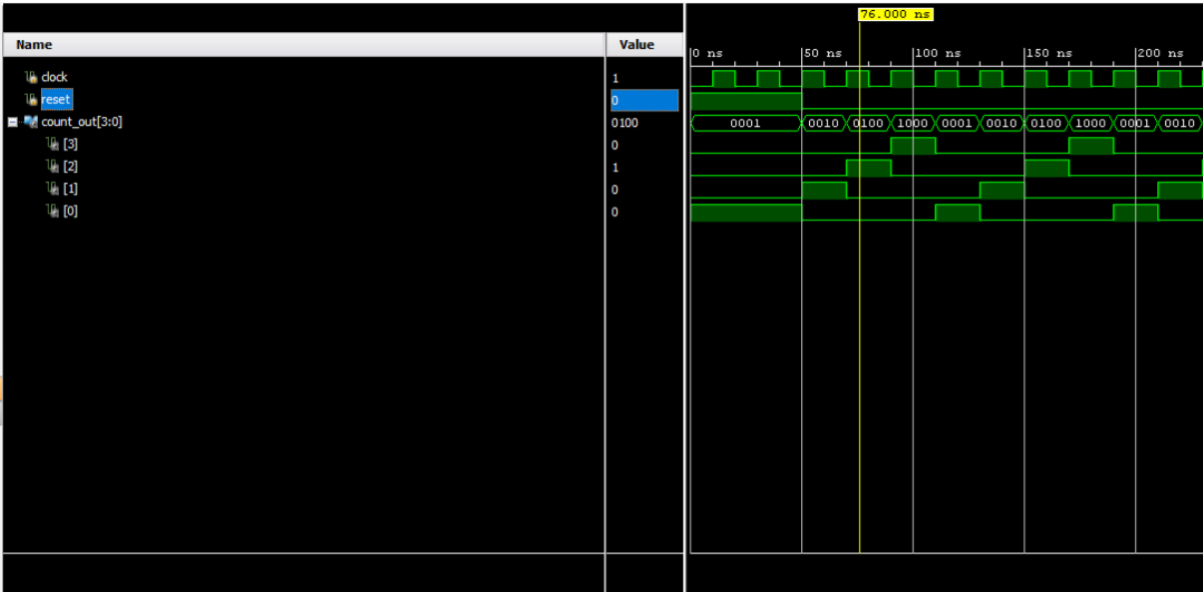



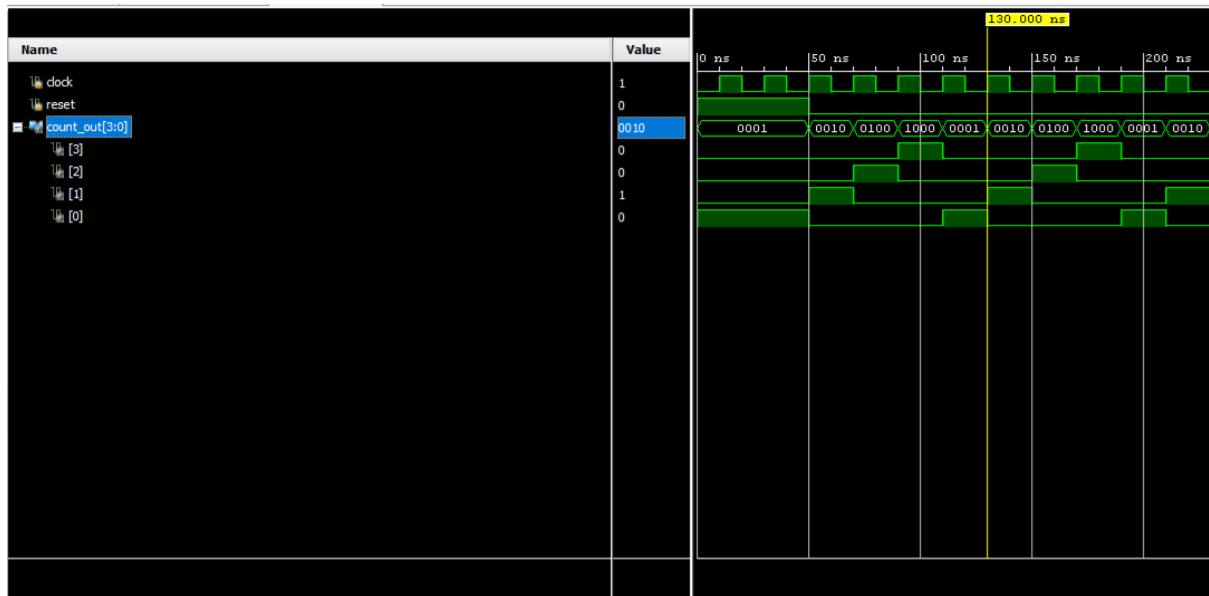


Johnson counter 4bit:

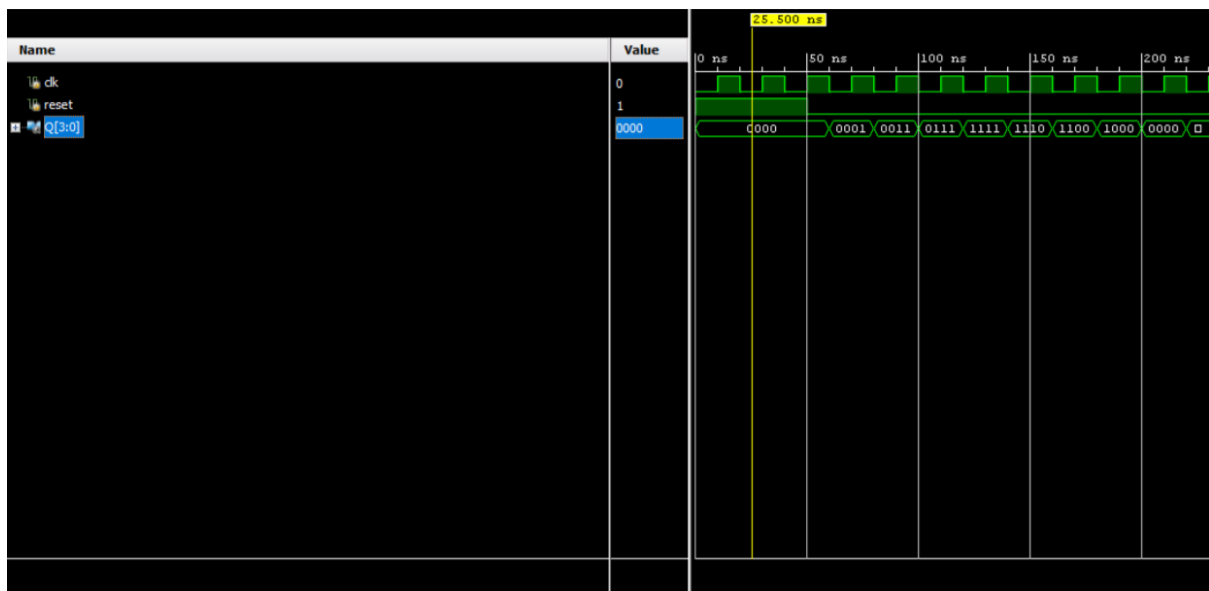

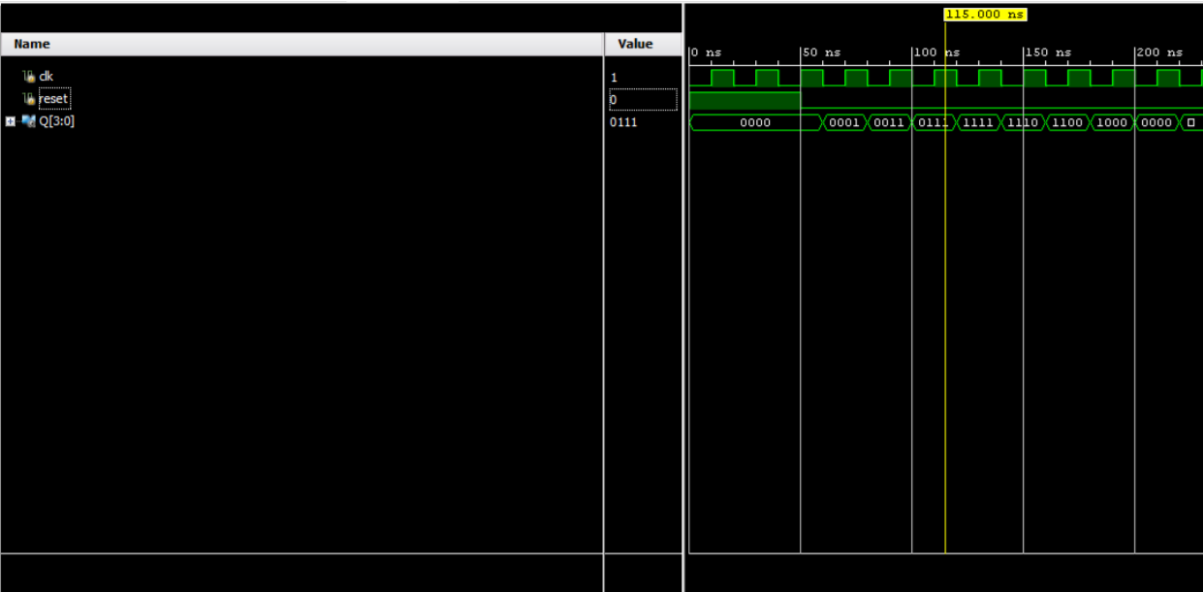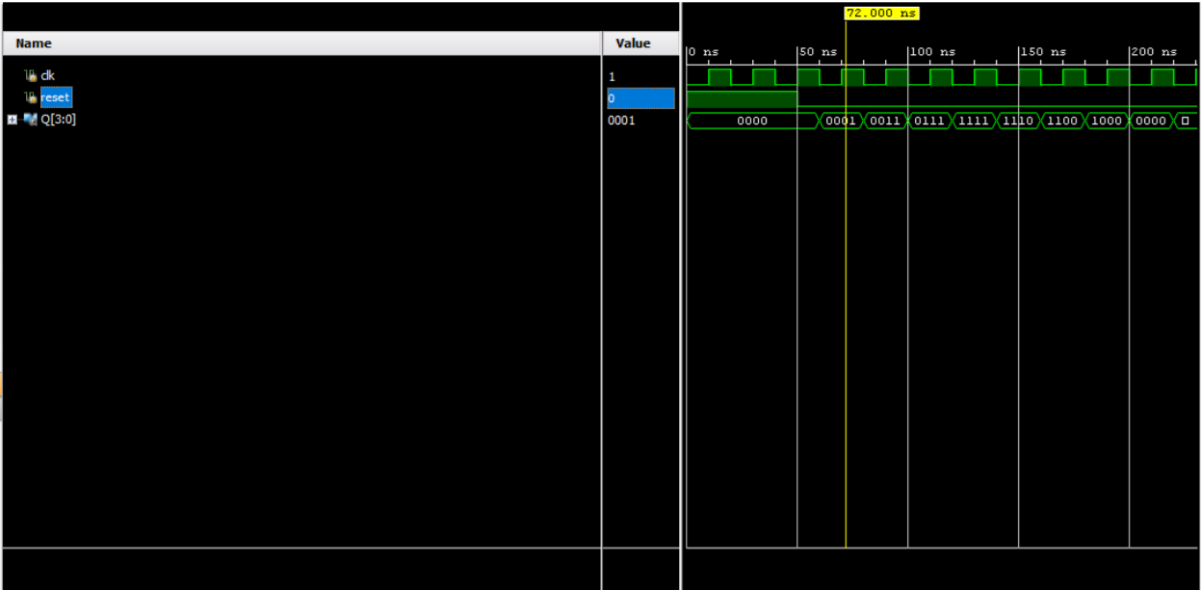



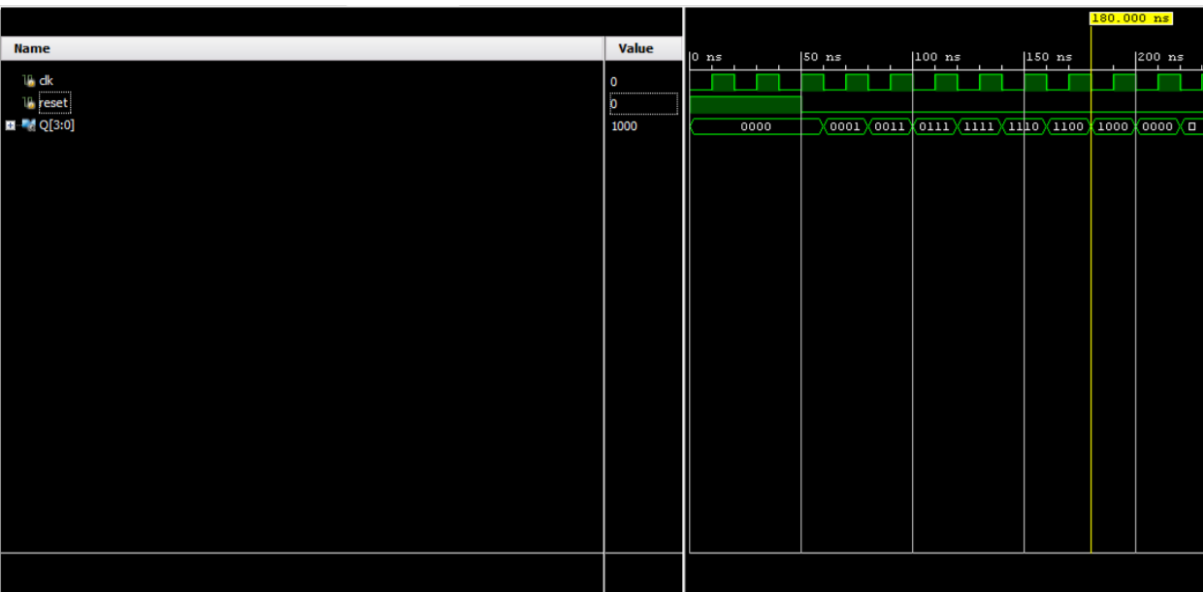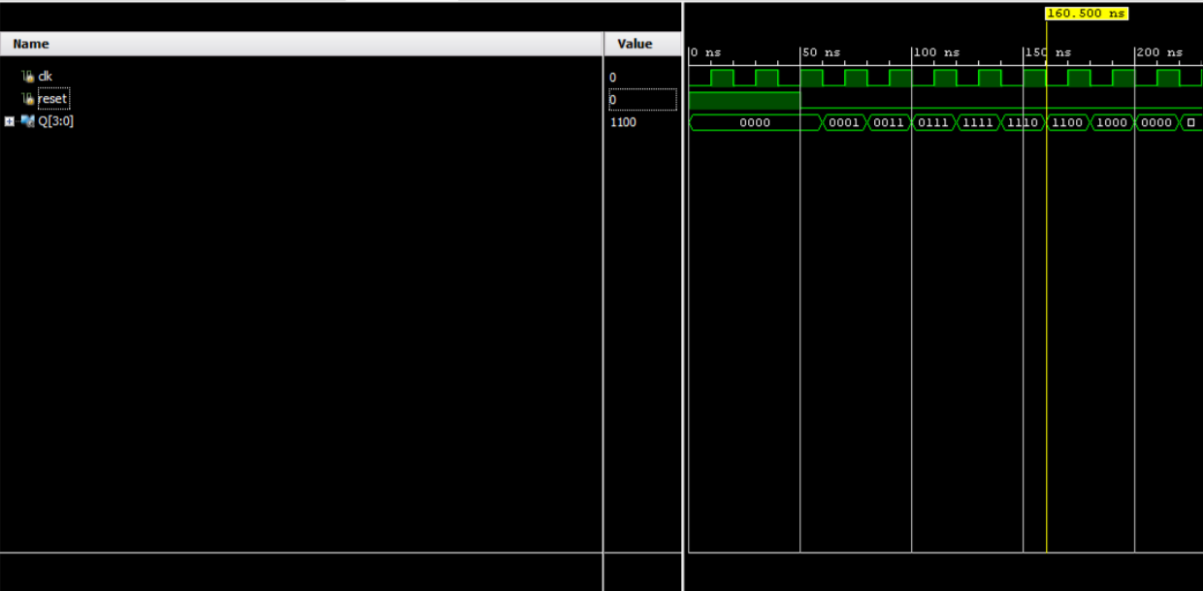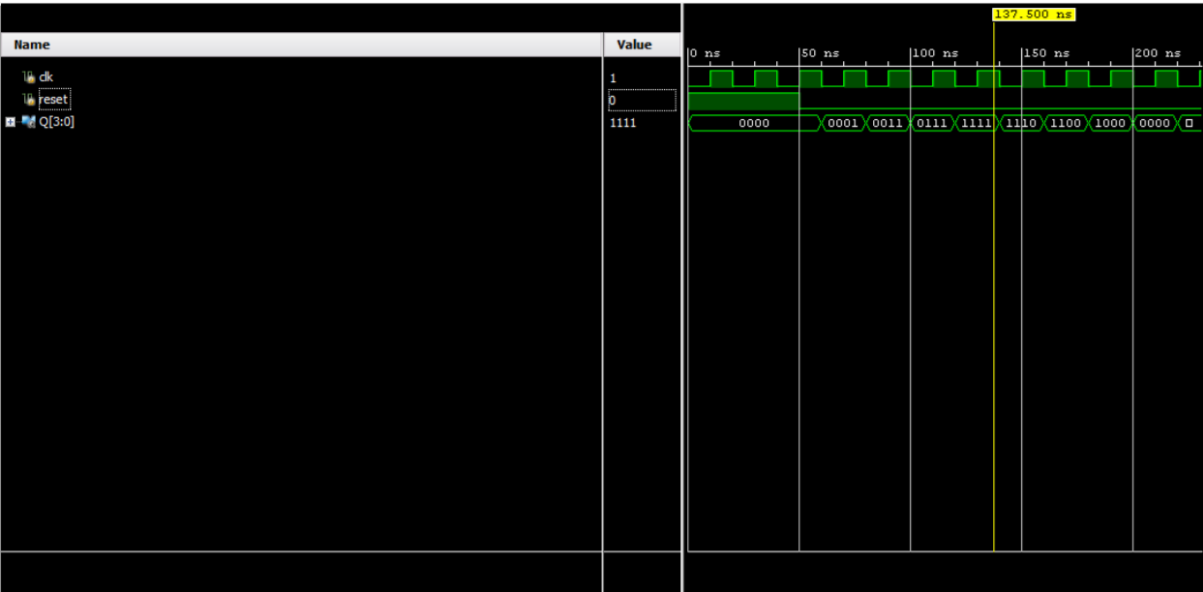

### Conclusion:

Now im able to design the logic and the timing diagrams and codes for ring and Jonhson counters (4-bit)