

DLD

EXPERIMENT - 9


Aim: To simulate the logic gates of 4-bit Synchronous Down counter

Tools used: vivado software

Truth table:

TRUTH TABLE											
P.S				N.S				OUTPUTS			
QD	QC	QB	QA	QD+	QC+	QB+	QA+	T D	TC	TB	TA
1	1	1	1	1	1	1	0	0	0	0	1
1	1	1	0	1	1	0	1	0	0	1	1
1	1	0	1	1	1	0	0	0	0	0	1
1	1	0	0	1	0	1	1	0	1	1	1
1	0	1	1	1	0	1	0	0	0	0	1
1	0	1	0	1	0	0	1	0	0	1	1
1	0	0	1	1	0	0	0	0	0	0	1
1	0	0	0	0	1	1	1	1	1	1	1
0	1	1	1	0	1	1	0	0	0	0	1
0	1	1	0	0	1	0	1	0	0	1	1
0	1	0	1	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	1	0	1	1	1
0	0	1	1	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	0	0	1	1
0	0	0	1	0	0	0	0	0	0	0	11
0	0	0	0	1	1	1	1	1	1	1	1

Diagram:

 

Expression:

$$TD = \sim QC \cdot \sim QB \cdot \sim QA$$

$$TC = \sim QB \cdot \sim QA$$

$$TB = \sim QA$$

$$TA = 1$$

Verilog codes:

```
module fourbit_syncdown(clk,in,count);
```

```
input clk,in;
```

```
output [3:0] count;
```

```
wire QA,QB,QC,QD,QA_bar,QB_bar,QC_bar,z1,z2;
```

```
tff t1(clk,in,QA,QA_bar);
```

```
tff t2(clk,QA_bar,QB,QB_bar);
```

```
andgate a1(QA_bar,QB_bar,z);
tff t3(clk,z,QC,QC_bar);
and_gate a2(z,QC_bar,z1);
tff t4(clk,z1,QD,QD_bar);
send s1(QA_bar,QB_bar,QC_bar,QD_bar,count);
endmodule

module send(a,b,c,d,out);
input a,b,c,d;
output [3:0] out;
assign out[0] = a;
assign out[1] = b;
assign out[2] = c;
assign out[3] = d;
endmodule

module tff(clk,in,out,out_bar);
input clk,in;
output out,out_bar;
reg out, out_bar;
initial
    out = 0;
always@(posedge clk)
begin
```

```
if(in == 1) begin
out = ~out;
out_bar = ~out;
end
else
begin
out = out;
out_bar = ~out;
end
end
endmodule

module andgate(a,b,z);
input a,b;
output z;
assign z = a&b;
endmodule
```

Test bench code:

```
module tb_fourbit_syncdowncounter;
reg clk,in;
wire [3:0] count;
fourbit_syncdownnc1(clk,in,count);
```

```
initial
begin
  clk = 1'b0; in = 1'b0;
  #20 in = 1'b1;
end
always
begin
  #5 clk = ~clk;
end
endmodule


output:
```











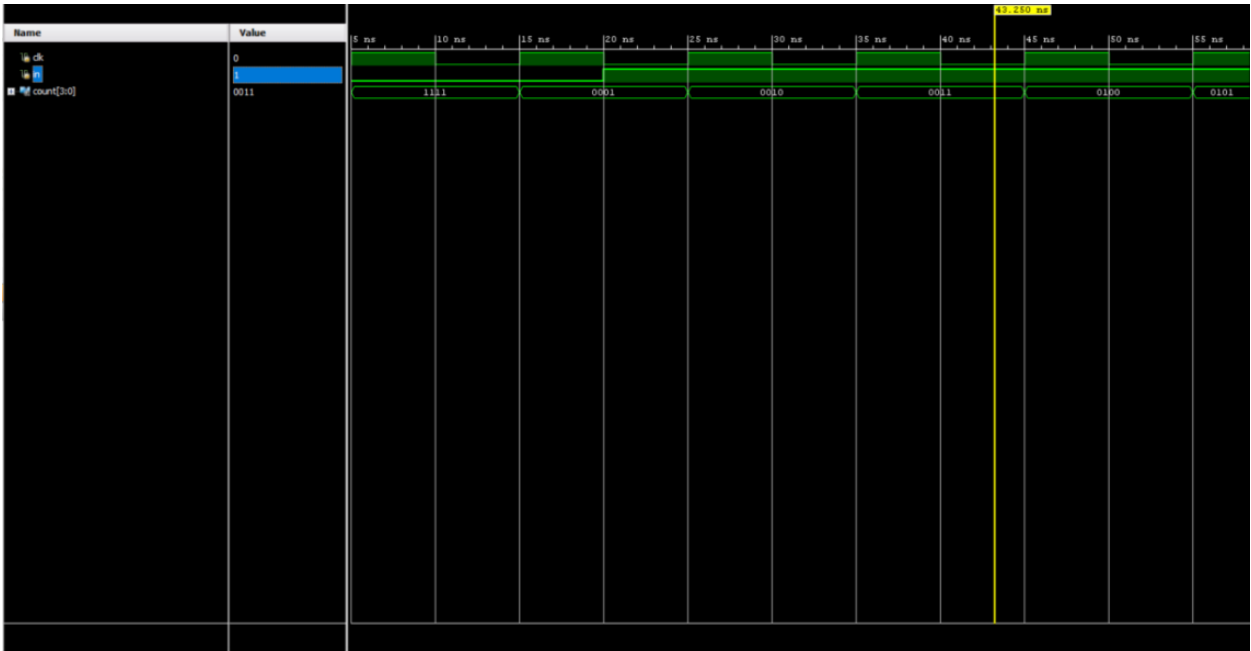

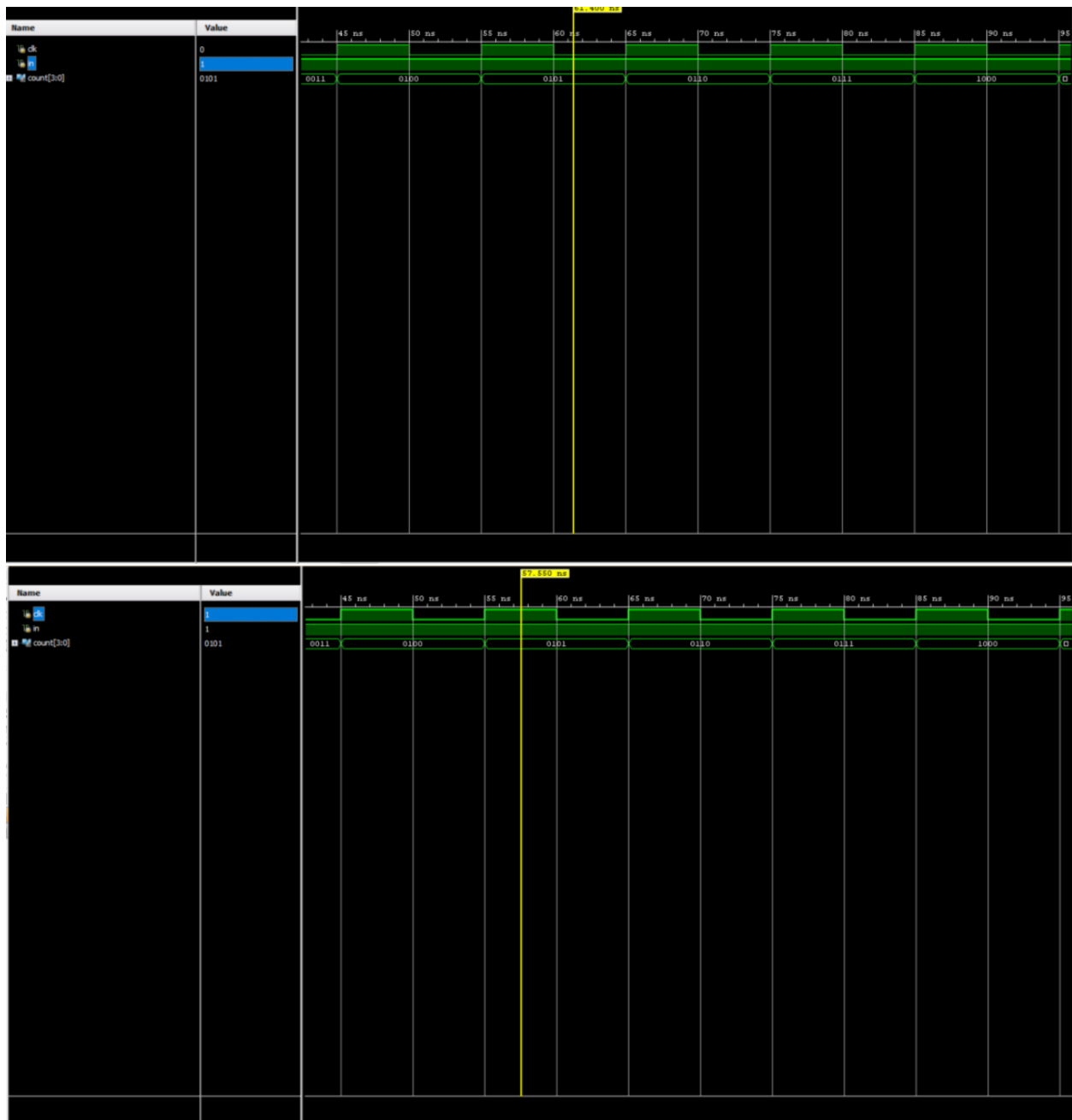

 

Conclusion:

Such that we can find the results of the codes with this software is very easy and fast and I came to know that sync 4 bit down counter Verilog code